



19/9/18

PAGE NO. : \_\_\_\_\_

DATE : / /
 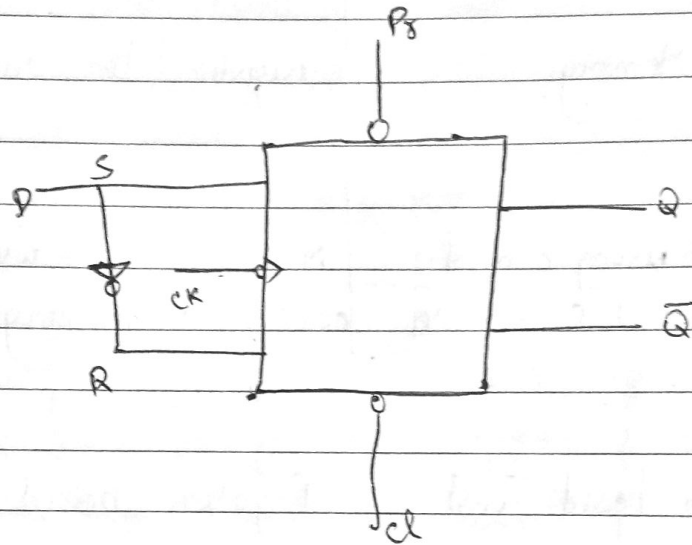
# Physics



D Flip-Flop → If input of clocked R-S Flip flop is connected with each other with the help of NOT gate. The input for S & R will be 1, 0 or 0, 1 that FF is called D FF, because the transfer of data from input to output is delayed.



TRUTH TABLE

D	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	1
1	1	0

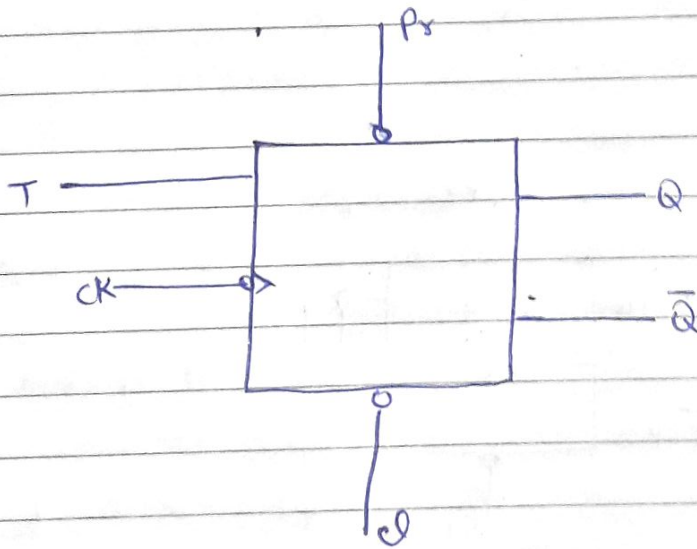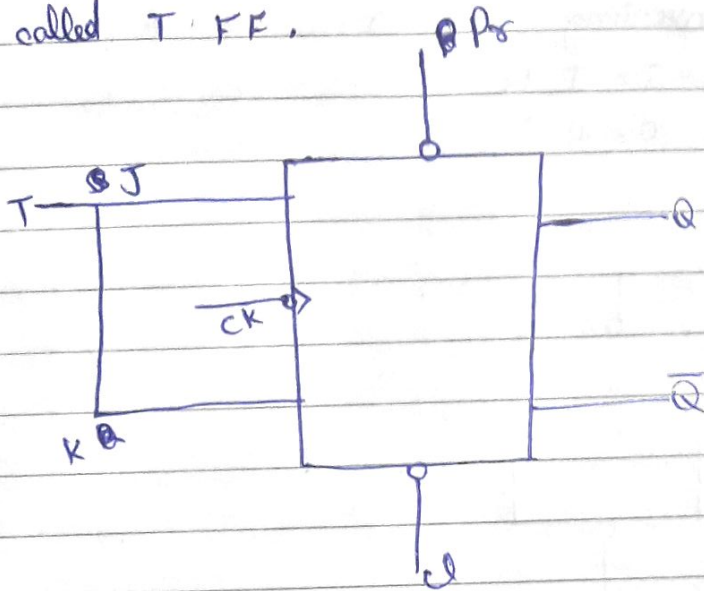T Flip Flip  $\rightarrow$  When inputs ~~J-K~~ <sup>J-K</sup> f.f connected with each other it behave like a toggle switch, so it is called T.FF.





Truth Table

T	$Q_{n+1}$	$\overline{Q}_{n+1}$
0	$Q_n$	$\overline{Q}_n$
1	$\overline{Q}_n$	$Q_n$

J-K Flip Flop → The uncertainty in the state of S-R flip flop i.e.  $S=R=1$  can be eliminated by converting into a J-K f.f.

$$S = J \cdot \bar{Q}$$

$$R = K \cdot Q$$

  


X

J	K	S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	0	0	$Q_n$	$\bar{Q}_n$
1	0	1	0	1	0
0	1	0	1	0	1
1	1	$\bar{Q}_n$	$Q_n$	$Q_n$	$\bar{Q}_n$

$J_n$	$K_n$	$Q_n$	$\bar{Q}_n$	$S_n$	$R_n$	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	0	1	0	0	$Q_n = 0$	$\bar{Q}_n$
0	0	1	0	0	0	$Q_n = 1$	$\bar{Q}_n$
1	0	0	1	1	0	1	0
1	0	1	0	0	0	1	0
0	1	0	1	0	0	0	1
0	1	1	0	0	1	0	1
1	1	0	1	1	0	$\bar{Q}_n$	$Q_n$
1	1	1	0	0	1	$Q_n$	$Q_n$

 Master slave J-K flip flop → It is a cascade of two S-R ff with feedback from the outputs of the second to the input of the first.



Master slave J-K f.f

Gate  $G_1, G_2, G_3$  &  $G_4$  form Master flip-flop the clock for Master flip-flop will be positive or positive edge triggered. Master flip-flop is same as J-K flip-flop. Output will be  $Q_m$  &  $\bar{Q}_m$ . When  $ck = 1$  master flip-flop is enabled & gives output  $Q_m$  &  $\bar{Q}_m$ .


$G_5, G_6, G_7$  &  $G_8$  form slave flip-flop. When  $ck = 1$  then clock for slave flip-flop  $\bar{ck} = 0$ . This time slave flip-flop is disabled.

When  $ck = 0$  master flip-flop is disabled and slave f.f is enabled. Slave flip-flop gives output after a pulse delay where master f.f. is operated. The input of slave f.f. is commanded by output of master f.f. The final output depends upon clock pulse given to Master flip-flop. Truth Table for Master & slave f.f. will be same as J-K f.f.

Master slave f.f. is designed to overcome race around difficulty, so that the uncertainty in output of J-K flip-flop is removed.

IC-7496

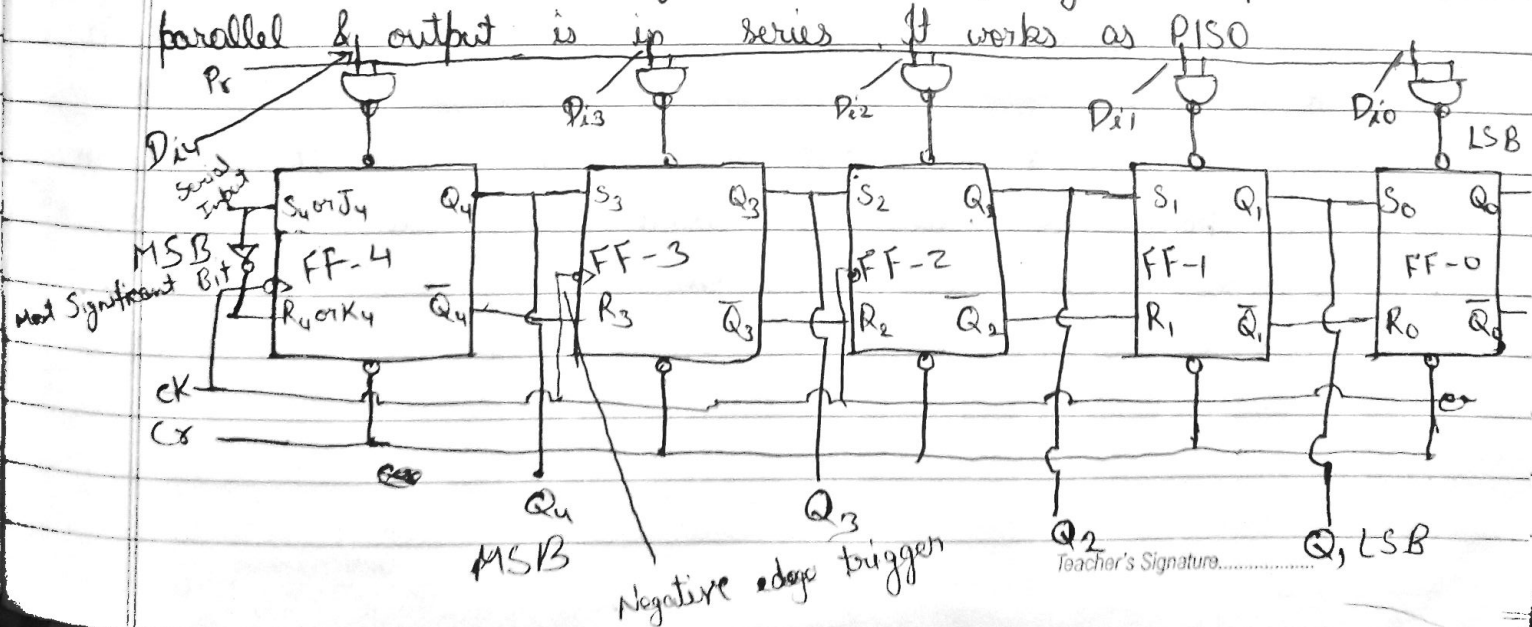Shift Register  $\rightarrow$  A five bit shift register is made of Master slave f.f. For this shift register inputs are parallel & output is in series. It works as PISO.




→ Negative edge triggered

→ Positive edge triggered

PAGE NO. :

DATE: / /

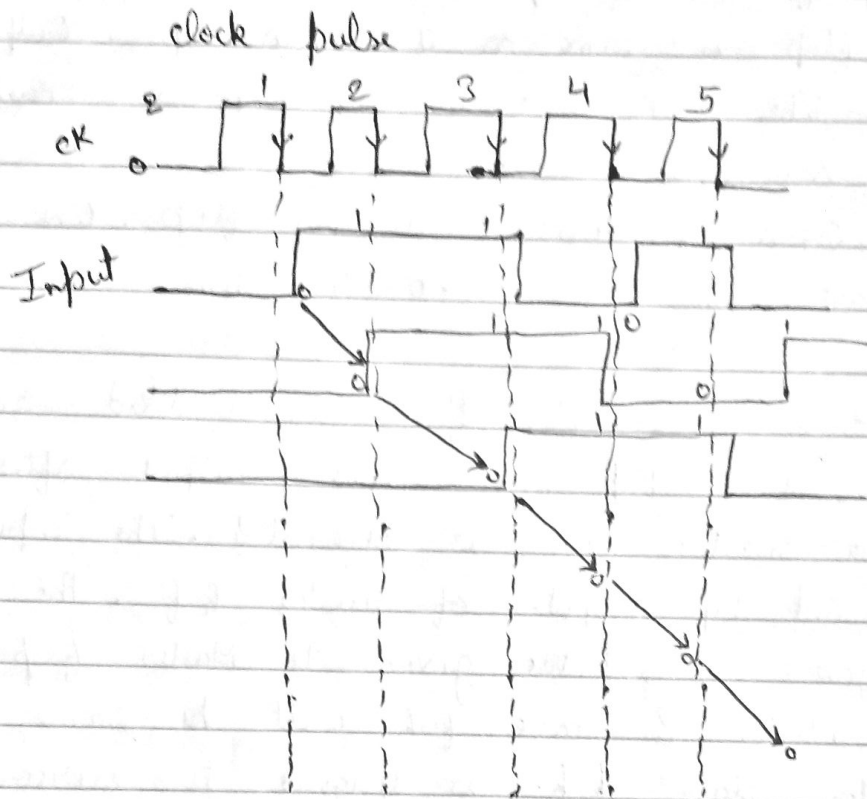Waveform of shift register for serial input →





Synchronous Counter & Asynchronous Counter → If all flip-flops in a counter are not clocked simultaneously that counter is called ripple counter.

If all flip-flops are clocked simultaneously that counter is called synchronous counter.

A circuit used for counting the pulse is known as counter.

If the no of state in counter is  $N$ . It is known as Modulo  $N$  counter & divide by  $N$  counter, for ring counter  $N$  state is known as modulo  $N$  but other counter known as  $2N$  Modulo counter.

A 3-bit binary counter →

 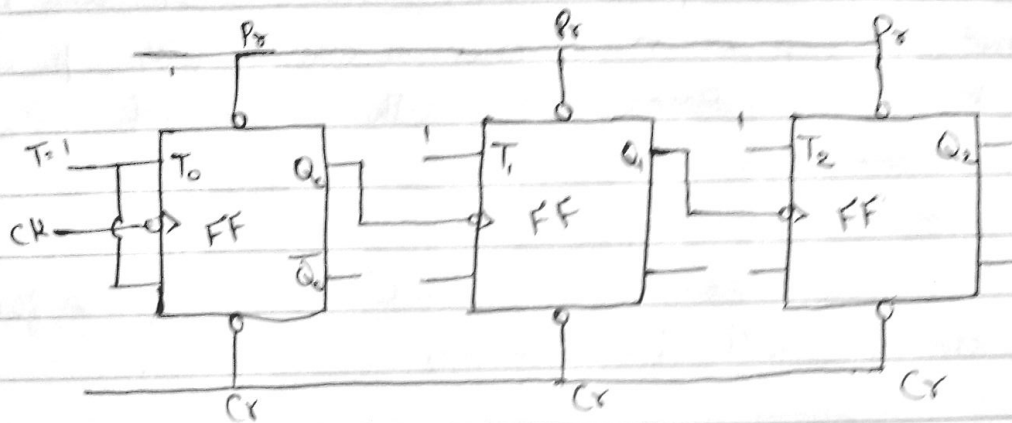

Ex of UP Counter

UP & DOWN Counter → If the output of counter increases with successive clock pulse, it is called an UP counter. It is triggered with negative edge clock.


If the output of counter decreases with successive clock pulse, it is called a DOWN counter. It is triggered with positive edge clock.

input  $H=0$  ] Negative Logic  
 $L=1$   
 input  $H=1$  ] Positive Logic  
 $L=0$

MOSFET  $\Rightarrow$  (Metal Oxide Semiconductor Field Effect Transistor)  $\Rightarrow$  MOSFET circuit is used due to high density of fabrication & low power dissipation. When MOSFET is used in devices circuit has p or n channel & circuit with p channel is known as PMOS. & with n channel is known as NMOS.

Charge carrier for p channel will be hole & for n channel will be electron

MOSFET inverter

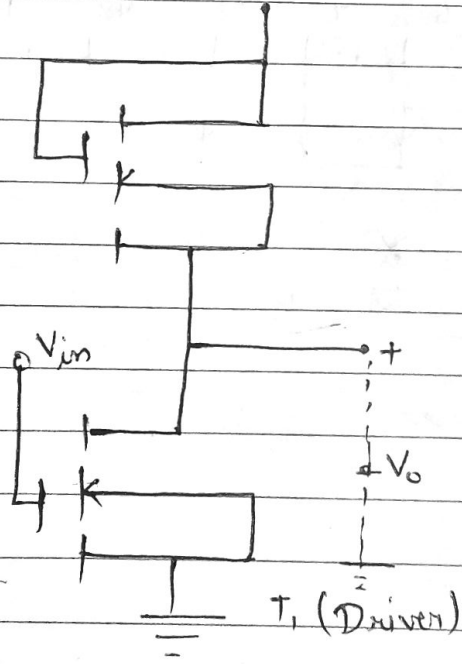

Most logic is used for design of LSI & VLSI ICs. It is not used for SSI & MSI. Most of the microprocessor memories & peripheral devices formed by MOSFET circuit.